

Tensor Decomposition For Logic Circuits

Ali Fele Paranj

February 6, 2025

Let A represent a boolean variable. Then observe that

$$A + \bar{A} = 1.$$

We can use this fact to simplify the logical circuits. For instance to implement $f(A, B, C, D) = \bar{A}BCD + A\bar{B}CD$ as it is we need more logic gates to implement its equivalent $f(A, B, C, D) = CD$. Karnaugh map makes such simplification possible for any logic function. For instance, consider the following truth table:

A	B	C	D	F(A,B,C,D)
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

We can write this function as

$$F(A, B, C, D) = \bar{A}BC\bar{D} + \bar{A}BCD + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD.$$

To decompose 4-linear form and then use the identity above simplify the function we can use the Karnaugh map.

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	0	0	0	1
	11	1	1	0	1
	10	1	1	1	1

The grouped boxes above shows which terms can be grouped to make a simpler term. For instance, the green box above show the following terms that can be grouped easily:

$$\begin{aligned}
 & ABC\overline{D} + AB\overline{C}D + A\overline{B}CD + A\overline{B}C\overline{D} \\
 &= ABC\overline{D} + AB\overline{C}D + A\overline{B}C\overline{D} + A\overline{B}CD \\
 &= AC\overline{D}(B + \overline{B}) + A\overline{B}C\overline{D}(D + \overline{D}) \\
 &= AC\overline{D} + A\overline{B}C\overline{D} \\
 &= AC\overline{D}.
 \end{aligned}$$

With a similar reasoning, the red box results in the term $A\overline{B}$ and the yellow box results in the term $BC\overline{D}$. So the simplified function will be

$$F(A, B, C, D) = AC\overline{D} + A\overline{B} + BC\overline{D}.$$